



SIDDARTHA INSTITUTE OF SCIENCE AND TECHNOLOGY:: PUTTUR

Siddharth Nagar, Narayanavanam Road – 517583

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

Subject with Code :STLD (19EC0401)

Course & Branch: B.Tech - ECE

Year & Sem: I B.Tech & II Sem

Regulation: R19

UNIT –I

Binary Systems, Boolean Algebra And Logic Gates

1. Convert the given decimal number 234 to binary, quaternary, octal, hexadecimal and BCD equivalent. **12M**
2. Convert the following to Decimal and then to Octal **12M**
 - i) 1234_{16} ii) $12EF_{16}$ iii) 10110011_2 iv) 352_6 v) 999_{16}
3. How are negative numbers represented? Represent signed numbers from +7 to -8 using different ways of representation. **12M**
4. a) Obtain the truth table for the Boolean function, $F = (A+B)(B+C)$ and express the function as sum of minterms and product of maxterms. **6M**
 b) Simplify the following Boolean functions to minimum number of literals **6M**
 - i) $XYZ + X'Y + XYZ'$ ii) $XZ + X'YZ$.
5. a) Simplify the following Boolean expressions to minimum no. of literals. **6M**
 - i) $ABC + A'B + ABC'$ ii) $(BC' + A'D)(AB' + CD')$
 b) Perform the following **6M**
 - i) Subtraction by using 10's complement for the given $3456 - 245$.
 - ii) Subtraction by using 2's complement for the given $111001 - 1010$.
6. a) With an example, explain in detail about the different types of binary codes. **8M**
 b) Convert the following to Decimal and then to Hexadecimal. **4M**
 - i) $(1234)_8$ ii) $(11001111)_2$
7. a) Obtain the Dual of the following Boolean expressions. **8M**
 - i) $AB + A(B+C) + B'(B+D)$ ii) $A+B+A'B'C$
 - iii) $A'B + A'BC' + A'BCD + A'BC'D'E$ iv) $ABEF + ABE'F' + A'B'EF$
 b) Simplify the expression $XY + X'Z + YZ$ in to minimum literals. **2M**
 c) Convert the $A+BC$ into canonical form. **2M**
8. a) Determine the canonical product-of-sums representation of the following functions **6M**
 - i) $f(A,B,C) = C(A'+B)(A+B')$ ii) $f(A,B,C) = A(A'+B')(A'+C')$
 b) Perform the following using BCD arithmetic **6M**
 - i) $(79)_{10} + (177)_{10}$ ii) $(481)_{10} + (178)_{10}$
9. a) Discuss about the laws of Boolean algebra. **9M**
 b) Why NAND and NOR gate is called as universal gate **3M**
10. a) State De Morgan's theorem and Duality. List Boolean laws and their Duals. **8M**
 b) Give the truth table of logic gates. **4M**
11. a) Brief about the Digital Logic Gates **8M**
 b) Discuss about Integrated circuits. **4M**

UNIT –II

Gate Level Minimization

- 1 . Simplify the following expression using the K-map $F(A,B,C,D) = \Sigma(1,2,3,4,5,7,9,11,12,13,14)$ and implement using basic gates **12M**
2. a) Minimize the following Boolean function using K-Map **6M**
 $F(A, B, C, D) = \Sigma m(0, 2, 4, 6, 8, 10, 12, 14).$
 b) Realize it using NAND Gates. **6M**
3. Simplify the following Boolean function using K map: $F(A, B, C, D) = \Sigma(2, 4, 6, 10, 12);$
 $d(A, B, C, D) = \Sigma(0, 8, 9, 13)$ and realize it using basic gates **12M**
4. a) Simplify the following expression using the K-map for the 3-variable.
 $Y = AB'C + A'BC + A'B'C + A'B'C' + AB'C'$ **6M**
 b) Simplify the Boolean function $F(A,B,C,D) = \Sigma(1,3,7,11,15) + d(0,2,5)$ **6M**
5. Simplify the expression using K-map for the following Boolean function and implement using two-level logic minimization $F(A, B, C, D, E) = \Sigma(0,1,4,5,16,17,21,25,29)$ **12M**
6. a) Implement the following Boolean function using NOR gates $Y = (AB' + A'B)(C + D')$. **6M**
 b) Implement the following function using only NAND gates $G = (A + B).(C. D + E)$ **6M**
- 7.. Simplify the following Boolean expressions using K-map. **12M**
 $F(W,X,Y,Z) = XZ + W'XY' + WXY + W'YZ + WY'Z$
8. Simplify the following Boolean function in POS form using K-map and implement using basic gates
 $F(A,B,C,D) = \Pi_M(1,2,4,5,9,12,13,14)$ **12M**
9. Simplify the following Boolean function using Tabulation method **12M**
 $Y(A,B,C,D) = \Sigma(1,3,5,8,9,11,15)$
10. Simplify the following Boolean function, $f(W,X,Y,Z) = \Sigma m(2,6,8,9,10,11,14,15)$ using Quine-McClukey tabular method **12M**
11. Simplifying the following expression using tabulation technique. **12M**
 $F = \Sigma m(0,1,2,8,9,15,17,21,24,25,27,31)$

UNIT –III**Combinational Logic Circuits**

- | | |
|--|-----|
| 1. With an example, illustrate the analysis procedure of combinational circuits. | 12M |
| 2.a) Brief about the Step by step methods to design a Combinational Circuits. | 6M |
| b) Design & implement half Adder with truth table. | 6M |
| 3. a) Design & implement Full Adder with truth table. | 6M |
| b) Design & implement Full Subtractor with truth table. | 6M |
| 4. a) Design & implement the 4 bit binary Adder. | 6M |
| b) Design & implement half Subtractor with truth table. | 6M |
| 5.a) Design & implement a 4-bit Binary-to-Gray code converter. | 6M |
| b) Design a 4 bit binary-to-BCDcode converter | 6M |
| 6. a) a) Implement the following Boolean function using 8:1 multiplexer. | 6M |
| $F(A,B,C,D) = A'BD' + ACD + B'CD + A'C'D$. | |
| b) What is multiplexer? Construct 4*1 multiplexer with logic gates and truth table | 6M |
| 7. Explain Carry Look Ahead Adder circuit with the help of logic diagram. | 12M |
| 8. a) Construct a BCD Adder-circuit. | 5M |
| b) Discuss in detail about serial adder with diagram | 7M |
| 9. Implement 4-bit Magnitude Comparator and write down its design procedure. | 12M |
| 10. a) Design & implement Full Adder using Decoder. | 5M |
| b) Implement a 2-bit Magnitude comparator . | 7M |
| 11. a)What is encoder? Design octal to binary encoder. | 7M |
| b) Design a 1:4 Demultiplexer and mention the applications of a DEMUX. | 5M |

UNIT –IV

Sequential Logic Circuits

1. a) Design D Flip Flop by using SR Flip Flop and draw the timing diagram. **6M**
 b) Write the differences between combinational and sequential circuits. **6M**
2. a) Draw the logic symbol, characteristics table and derive characteristics equation of JK flip flop. **6M**
 b) Design T Flip Flop by using JK Flip Flop and draw the timing diagram. **6M**
3. a). With logic diagram and timing diagram discuss about SR Flip Flop. **12M**
4. a) Convert S-R flip flop into JK-flip flop. Draw and explain the logic diagram. **6M**
 b) Draw the circuit of JK flip flop using NAND gates and explain its operation **6M**
5. Explain about state table, state diagram and state assignment techniques with an example. **12M**
6. Design and implement 3-bit ripple counter using J-K flip flop. Draw the timing diagram. **12M**
7. With a neat sketch explain MOD 6 Johnson counter using D FF. **IES 2015** **12M**
8. Explain about different types of shift registers. Briefly describe its operation. **12M**
9. What are the different types of counters .Explain briefly. **12M**
- 10.a) Write the difference between Latch and Flip flop **2M**
 b) List asynchronous inputs of a sequential device **2M**
 c) Draw the block diagram of sequential circuit using combinational circuit and memory unit. **2M**
 d) Draw the logic circuit of flip-flop and truth table using NOR gates. **2M**
 e) Give the comparison between combinational circuits and sequential circuits. **2M**
 f) What is the advantage of choosing D flip flop in sequential circuits **2M**

UNIT –V
Finite State Machines and Programmable Memories

1. Explain different types of memory devices. 12M
2. Realize $F = \Sigma m(0,2,3,7,9,11,15,16)$ using ROM 12M
3. Implement the following Boolean function using PLA 12M
(i) $F(w,x,y,z) = \Sigma m(0,1,3,5,9,13)$ (ii) $F(w,x,y,z) = \Sigma m(0,2,4,5,7,9,11,15)$
4. Implement the following Boolean function using PAL. 12M
(i) $A(w,x,y,z) = \Sigma m(0,2,6,7,8,9,12,13)$ (ii) $B(w,x,y,z) = \Sigma m(0,2,6,7,8,9,12,13,14)$
(iii) $C(w,x,y,z) = \Sigma m(1,3,4,6,10,12,13)$ (iv) $D(w,x,y,z) = \Sigma m(1,3,4,6,9,12,14)$
5. Explain in detail about Content Addressable memory structure and its function. 12M
6. Implement the following Boolean function using PLA 12M
(i) $F_1 = \Sigma m(0,1,2,3,8,10,12,14)$ (ii) $F_2 = \Sigma m(0,1,2,3,4,6,8,10,12,14)$.
7. a) How does the PLDs differ from fixed logic devices? What are the primary advantages of using PLDs. 6M
b) Implement PLA circuit for the following functions $F_1(A,B,C) = \Sigma m(3,5,6,7)$,
 $F_2(A,B,C) = \Sigma m(0,2,4,7)$. 6M
8. Differentiate among ROM, PROM, DROM, EPROM, EEPROM, RAM. 12M
9. Give the logic implementation of a 32x4 bit ROM using a decoder of a suitable figure. 12M
10. Draw the diagram of mela type FSM for serial adder.. 12M
11. a) Give the classification of semiconductor memories. 2M
b) Draw a simple memory with necessary signals. 2M
c) What are the advantages of flash memory? 2M
d) What is the concept of CCD? 2M
e) Compare PAL, PLA & ROM 2M
f) Distinguish between mela & moore machines. 2M