



**SIDDHARTH GROUP OF INSTITUTIONS :: PUTTUR  
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

**QUESTION BANK (DESCRIPTIVE)**

**Subject with Code:** Electronic Devices and Circuits (19EC0402) **Course & Branch:** B. Tech - ECE

**Year & Sem:** II-B. Tech & I-Sem

**Regulation:** R19

**UNIT –I**  
**PN JUNCTION DIODE**

1. a) Define cut in voltage of a PN Junction diode and give its values for Si and Ge diodes. [L1][CO1][4M]  
b) Illustrate the action of PN junction diode under forward bias and reverse bias and sketch its V-I Characteristics. [L2][CO1][6M]
2. a) Analyze the current components in a PN diode and determine the expression for diode current equation. [L4][CO1][6M]  
b) When a reverse bias is applied to a germanium PN junction diode, the reverse saturation current at room temperature is  $0.3\mu\text{A}$ . Determine the current flowing in the diode when  $0.15\text{V}$  forward bias is applied at room temperature. [L5][CO4][4M]
3. a) The reverse saturation current of a silicon PN junction diode is  $10\mu\text{A}$ . Solve the diode current for the forward bias voltage of  $0.6\text{V}$  at  $25^\circ\text{C}$ . [L3][CO4][4M]  
b) Demonstrate the effect of temperature on V-I characteristics of PN junction diode. [L2][CO1][6M]
4. a) Draw the ideal diode characteristics and give its circuit symbol. [L1][CO1][4M]  
b) A p-n junction germanium diode has a reverse saturation current of  $0.10\mu\text{A}$  at the room temperature of  $27^\circ\text{C}$ . It is observed to be  $30\mu\text{A}$ , when the room temperature is increased. Calculate the new room temperature. Also determine the current passing through the diode at this new temperature. [L5][CO4][6M]
5. a) Explain about Diode resistances and determine the expression for forward dynamic resistance. [L2][CO1][6M]  
b) Examine the forward resistance of a PN junction diode when the forward current is  $5\text{mA}$  at  $T = 300\text{K}$ . Assume Silicon diode. [L4][CO4][4M]
6. a) Define Transition and Diffusion capacitances of a PN Junction Diode. [L1][CO1][4M]  
b) Determine the expression for transition capacitance of a PN Junction Diode. [L5][CO1][6M]
7. a) List the application of PN junction and Zener diodes. [L1][CO1][4M]  
b) Determine the expression for Diffusion capacitance of a PN Junction Diode. [L5][CO1][6M]
8. a) Define Breakdown voltage and give the circuit symbol for Zener Diode. [L1][CO1][4M]  
b) Infer the Breakdown mechanisms in PN Junction Diode. [L2][CO1][6M]
9. a) Mention the importance of Diode Clipper and list its applications. [L2][CO1][4M]  
b) Draw and explain the V-I characteristics of Zener diode. Show that the Zener diode can act as a voltage regulator with a neat diagram. [L1][CO5][6M]
10. a) Construct the Positive and Negative Diode Clippers with neat waveforms. [L3][CO5][5M]  
b) What is a Clamper circuit? Describe about positive and negative clampers with neat circuit diagrams. [L1][CO5][5M]

**UNIT –II**  
**RECTIFIERS, FILTERS AND SPECIAL PURPOSE DEVICES**

1. a) Draw the circuit diagram of a half wave rectifier and explain its operation with the help of waveforms. [L1][CO1][5M]  
b) Inspect the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power input of a Half Wave Rectifier. [L4][CO1][5M]
2. a) Draw the circuit diagram of a Full wave rectifier and with the help of waveforms describe its operation. [L1][CO1][5M]  
b) Determine the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power input of a Full Wave Rectifier. [L5][CO1][5M]
3. a) A half wave rectifier is supplied from a 230V, 50 Hz supply with a step-down ratio of 3:1 to a resistive load of 10k $\Omega$ . The diode forward resistance is 75 $\Omega$  while transformer secondary is 10 $\Omega$ . Examine maximum, average, RMS values of current, DC output voltage, efficiency of rectification and ripple factor. [L4][CO1][5M]  
b) A full wave rectifier circuit is fed from a transformer having a center-tapped secondary winding. The rms voltage from either end of secondary to center tap is 30V. If the diode forward resistance is 2 $\Omega$  and that of the half secondary is 8 $\Omega$ , for a load of 1 K $\Omega$ . Solve DC power delivered to the load, efficiency of rectification and TUF of secondary. [L3][CO2][5M]
4. a) With neat circuit diagram and waveforms, illustrate the construction and working of Bridge rectifier. [L2][CO1][5M]  
b) A 5K $\Omega$  load is fed from a bridge rectifier connected across a transformer secondary whose primary is connected to 460V, 50 Hz supply. The ratio of number of primary turns to secondary turns is 2:1. Estimate dc load current, ripple voltage and PIV rating of diode. [L5][CO4][5M]
5. a) Draw the circuit diagram of Full wave rectifier with inductor filter and illustrate its operation. Also derive the expression for ripple factor. [L1][CO3][5M]  
b) Find the value of inductance to be used in the inductor filter connected to a full wave rectifier operating at 60 Hz to provide a dc output with 4% ripple for a 100 $\Omega$  load. [L1][CO2][5M]
6. a) With neat circuit diagram and waveforms, Explain the operation of Full wave rectifier with capacitor Filter and determine the expression for its ripple factor. [L2][CO3][5M]  
b) Inspect the value of capacitance to be used in a capacitor filter connected to a full wave rectifier operating at a standard aircraft power frequency of 400 Hz, if the ripple factor is 10% for a load of 500 $\Omega$ . [L4][CO2][5M]
7. a) Demonstrate the working principle of LC filter with neat diagram and derive the expression for its ripple factor. [L2][CO3][5M]  
b) Dissect the construction and working principle of CLC or  $\pi$  section filter along with derivation for its ripple factor. [L4][CO2][5M]
8. a) Recall a notes on Liquid Crystal Display and Illustrate dynamic scattering LCD and field effect LCD with neat diagram. [L1][CO3][5M]  
b) Extend the construction, working principle and characteristics of LED with neat diagram. Also list the and applications of LED. [L2][CO2][5M]
9. a) Explain the principle involved in working of Varactor diode and give its characteristics. [L2][CO5][5M]  
b) Explain the volt ampere characteristics of a Tunnel diode with the help of energy band diagrams and List its applications. [L2][CO5][5M]
10. a) Demonstrate the construction, working and characteristics of UJT with neat diagram. [L2][CO5][5M]  
b) Explain with diagram the construction, working and applications of Solar Cell. [L2][CO5][5M]


**UNIT –III**  
**TRANSISTOR CHARACTERISTICS: BJT & FET**

1. a) Interpret the operation of NPN transistor with diagram. [L2][CO1][5M]  
b) If the base current in a transistor is  $20\mu\text{A}$  when the emitter current is  $6.4\text{mA}$ , what are the values of  $\alpha$  and  $\beta$ ? Also calculate the collector current. [L1][CO4][5M]
- 2.a) Explain the current components of PNP transistor, the Emitter Efficiency, Base Transportation Factor and Large signal current gain. [L2][CO1][5M]  
b) With neat diagram, Interpret the Input and Output characteristics of a BJT in CB Configuration. [L2][CO5][5M]
3. Explain the Input and Output characteristics of a BJT in CE Configuration. Indicate the regions of operations in the output characteristics and list the applications in those regions. [L2][CO5][10M]
4. a) Illustrate the Input and Output characteristics of BJT in CC Configuration. [L2][CO5][6M]  
b) With a neat diagram, Explain how a transistor acts as an amplifier? [L2][CO1][4M]
5. a) Evaluate the relation between  $\alpha$ ,  $\beta$  and  $\gamma$  of a Transistor. [L5][CO1][5M]  
b) For a transistor, the leakage current is  $0.1\mu\text{A}$  in CB configuration, while it is  $19\mu\text{A}$  in CE configuration. Find  $\alpha$  &  $\beta$  of the same transistor? [L1][CO4][5M]
6. Explain the construction and working principle of N-channel JFET. [L2][CO1][10M]
7. a) Define the JFET Volt-Ampere Characteristics and determine FET parameters. [L1][CO1][5M]  
b) Compare the performance of BJT with FET. [L2][CO1][5M]
8. a) With the help of neat diagram, Explain the operation and characteristics of n-channel enhancement type MOSFET. [L2][CO5][8M]  
b) Categorize the difference between depletion and enhancement MOSFET. [L4][CO1][2M]
9. Interpret the operation and characteristics of n-channel depletion type MOSFET with diagram. [L2][CO5][10M]
10. a) Compare the performance of JFET with MOSFET. [L2][CO1][6M]  
b) List the applications of JFET and MOSFET. [L1][CO1][4M]


## UNIT- IV

### TRANSISTOR BIASING AND THERMAL STABILIZATION

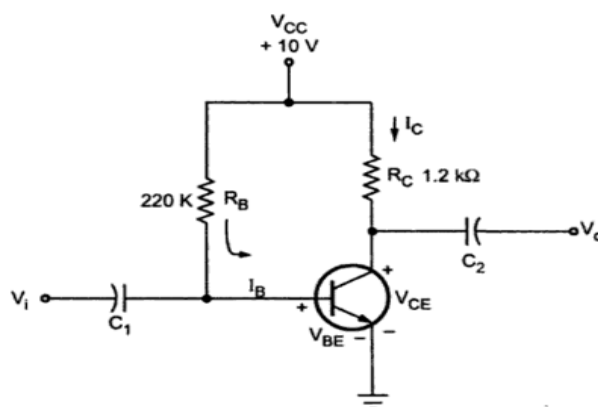
1. a) Define Transistor Biasing and explain the need for Biasing. [L1][CO3][5M]  
 b) Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. [L2][CO3][5M]
2. a) List the different types of Biasing a Transistor and explain the Fixed Bias of a Transistor [L4][CO6][5M]  
 b) Explain Collector to Base bias of a Transistor with neat circuit diagram. [L2][CO6][5M]
3. a) Determine the expressions for the stability factors  $S$ ,  $S'$  and  $S''$  of a BJT Fixed bias. [L5][CO3][8M]  
 b) What are the disadvantages of fixed bias circuit of BJT? [L1][CO1][2M]
4. a) Define Stability Factor  $S$ . Derive the stability factor  $S$  for collector to base bias of BJT. [L1][CO6][5M]  
 b) Design a collector to base bias circuit for the specified conditions:  $V_{cc} = 15V$ ,  $V_{CE} = 5V$ ,  $I_C = 5mA$  and  $\beta = 100$ . [L6][CO2][5M]
5. Estimate the stability factors  $S$ ,  $S'$  and  $S''$  of a BJT Voltage Divider bias. [L5][CO6][10M]
6. a) For the circuit shown in the Figure, solve  $I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_B$ ,  $V_C$  and  $V_{BC}$ . Assume that  $V_{BE} = 0$  and  $\beta = 50$ . [L3][CO2][5M]



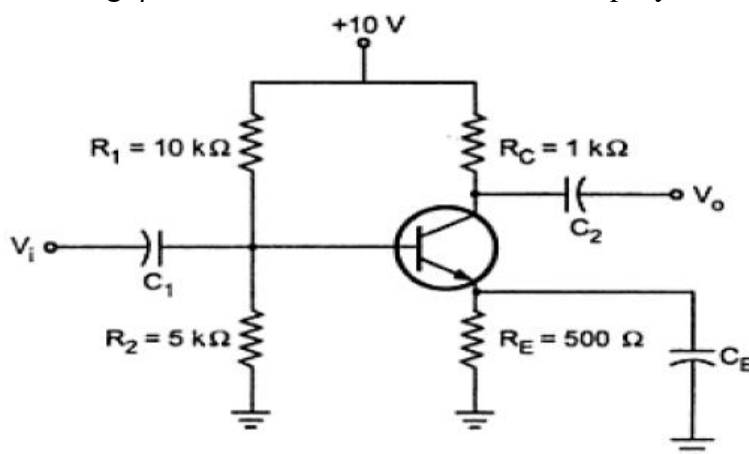- b) Interpret Diode Compensation Technique for the parameters  $V_{BE}$  and  $I_{CO}$ . [L2][CO3][5M]
7. a) Illustrate Thermistor Compensation Technique. [L2][CO3][4M]  
 b) For the circuit shown in Fig.  $\beta = 100$  for the silicon transistor. Simplify  $V_{CE}$  and  $I_C$ . [L4][CO2][5M]




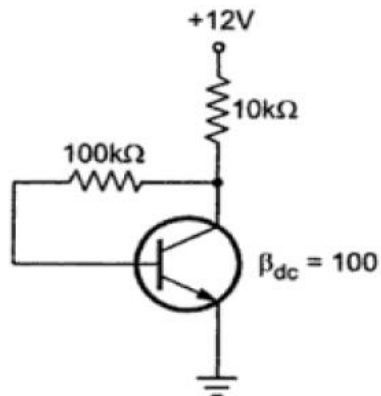8. a) Explain Thermal Runaway and Thermal Resistance. [L2][CO3][5M]  
 b) Solve the Q-point values for the circuit shown in the Fig. [L3][CO2][5M]



9. Draw the dc load line for the following transistor configuration. Obtain the quiescent Point.

[L1][CO2][10M]

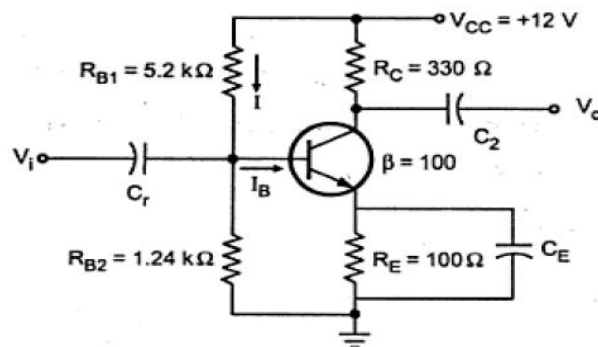

10. a) Dissect Sensistor Compensation Technique.  
b) Estimate the condition for achieving Thermal Stability.


[L4][CO3][4M]

[L5][CO3][6M]


## UNIT- V

### SMALL SIGNAL LOW FREQUENCY TRANSISTOR AMPLIFIER

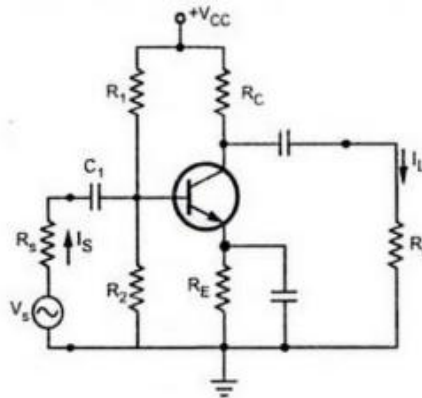1. a) Discuss the frequency response of an amplifier. [L6][CO1][4M]  
 b) Why hybrid model is used for the analysis of BJT amplifier at low frequencies? Draw the hybrid model for CE transistor and derive the hybrid parameters. [L1][CO1][6M]
2. Using low frequency h-parameter model, Evaluate the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration. [L5][CO3][10M]
3. a) With neat diagram, Summarize the parameters of CE amplifier using approximate analysis. [L2][CO3][5M]  
 b) Examine the expressions for current gain, voltage gain, input impedance and output impedance of CB amplifier using simplified hybrid model. [L4][CO3][5M]
4. a) Determine the parameters  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_o$  of Common Collector Amplifier using simplified hybrid model analysis. [L5][CO3][5M]  
 b) A voltage source of internal resistance,  $R_s = 900\Omega$  drives a CC amplifier using load resistance  $R_L = 2000\Omega$ . The CE h parameters are  $h_{fe} = 60$ ,  $h_{ie} = 1200\Omega$ ,  $h_{oe} = 25\mu A/V$  and  $h_{re} = 2 \times 10^{-4}$ . Solve  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_o$  using approximate analysis. [L3][CO2][5M]
5. A CE amplifier is driven by a voltage source of internal resistance  $R_s = 800\Omega$  and the load impedance of  $R_L = 1000\Omega$ . The h-parameters are  $h_{ie} = 1k$ ,  $h_{fe} = 50$ ,  $h_{oe} = 25\mu A/V$  and  $h_{re} = 2 \times 10^{-4}$ . Find current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. [L1][CO2][10M]
6. For a CB transistor amplifier driven by a voltage source of internal resistance  $R_s = 1200\Omega$ , the load Impedance of  $R_L = 1000\Omega$ . The h parameters are  $h_{ib} = 22\Omega$ ,  $h_{rb} = 3 \times 10^{-4}$ ,  $h_{fb} = -0.98$ ,  $h_{ob} = 0.5\mu A/V$ . Find current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. [L1][CO2][10M]
7. Consider a single stage CE amplifier with  $R_s = 1k\Omega$ ,  $R_1 = 50k\Omega$ ,  $R_2 = 2k\Omega$ ,  $R_c = 1k\Omega$ ,  $R_L = 1.2k\Omega$ ,  $h_{fe} = 50$ ,  $h_{ie} = 1.1k$ ,  $h_{oe} = 25\mu A/V$  and  $h_{re} = 2.5 \times 10^{-4}$ , as shown in Fig. Solve  $A_i$ ,  $R_i$ ,  $A_v$ ,  $A_{vs}$ ,  $A_{is}$  and  $R_o$ . [L3][CO2][10M]



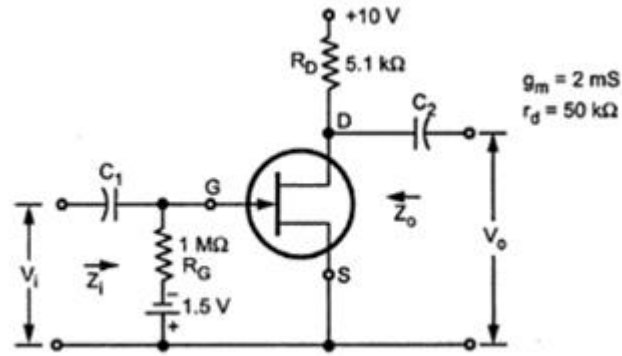8. a) Develop the expression for current gain, voltage gain, input impedance and output impedance for Common Emitter Amplifier with Emitter Resistor using simplified hybrid model. [L3][CO3][5M]  
 b) A CE amplifier is driven by a voltage source of internal resistance  $R_s = 1000\Omega$  and the load impedance of  $R_L = 2k\Omega$ . The h-parameters are  $h_{ie} = 1.3k$ ,  $h_{fe} = 55$ ,  $h_{oe} = 22\mu A/V$  and  $h_{re} = 2 \times 10^{-4}$ . Neglecting biasing resistors, Estimate the value of current gain, voltage gain, input impedance, output impedance for the value of Emitter Resistor  $R_E = 200\Omega$  inserted in the emitter circuit. [L5][CO2][5M]
9. a) For the circuit shown in Figure below, Determine input impedance, output impedance and voltage gain. [L5][CO5][5M]



- b) Label the circuit diagram of JFET Common Source amplifier with voltage divider bias for bypassed  $R_s$  and determine the expression for input impedance, output impedance and voltage gain. [L1][CO6][5M]
10. Summarize the expressions for input impedance, output impedance and voltage gain of JFET Common Drain amplifier with neat diagram. [L2][CO5][10M]